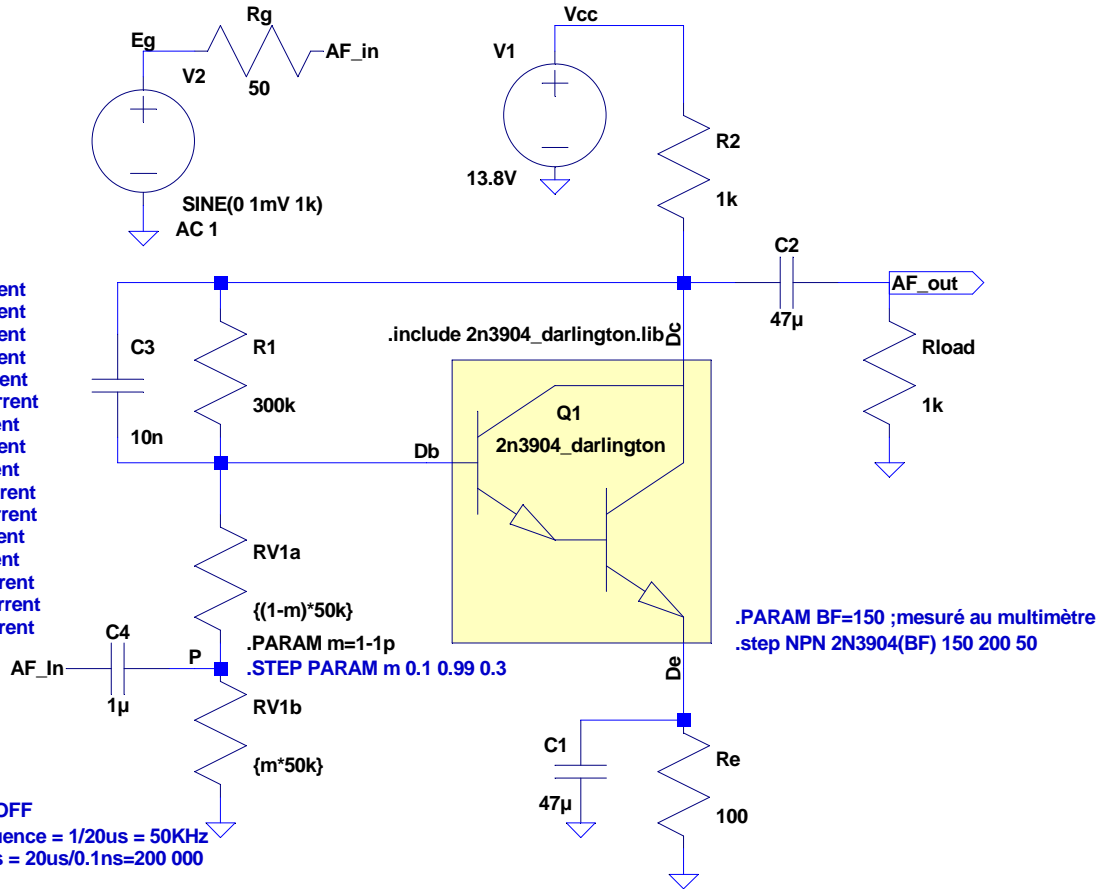


TRANSCEIVER CW F8EOZ - Audio Amplifier - Darlington pair stage - V 30/12/2012 12:40

--- Operating Point ---

V(vcc):	13.8	voltage
V(p):	1.48705	voltage
V(db):	1.48705	voltage
V(de):	0.278174	voltage
V(dc):	10.9866	voltage
V(eg):	0	voltage
V(af_in):	7.43527e-017	voltage
V(af_out):	5.16371e-013	voltage
I(C3):	9.49957e-020	device_current
I(C2):	5.16371e-016	device_current
I(C4):	1.48705e-018	device_current
I(C1):	1.30742e-017	device_current
I(Rg):	-1.48705e-018	device_current
I(Rload):	5.16371e-016	device_current
I(R2):	0.00281338	device_current
I(R1):	3.16652e-005	device_current
I(Re):	0.00278174	device_current
I(Rv1a):	3.16397e-005	device_current
I(Rv1b):	3.16394e-005	device_current
I(V2):	1.48705e-018	device_current
I(V1):	-0.00281338	device_current
Ix(q1:C):	0.00278171	subckt_current
Ix(q1:B):	2.56506e-008	subckt_current
Ix(q1:E):	-0.00278174	subckt_current



;noise V(AF_out) V2 dec 10001 10 10Meg

.net I(Rload) V2

.options plotwinsize=0

;tran 0 10000us 0 50.0ns

.ac dec 10001 10 100k

;op

Data compression OFF

Résolution de fréquence = 1/20us = 50KHz

Nombre d'exemples = 20us/0.1ns=200 000